

How many different numbers can be represented with 30 bits?

- ☐ (4294967295)₁₀
- ☐ (4294967296)₁₀
- ☒ (1073741824)₁₀
- ☐ (1073741823)₁₀

What is the largest unsigned 30-bit binary number?

- ☐ (4294967295)₁₀
- ☐ (4294967296)₁₀
- ☐ (1073741824)₁₀
- ☒ (1073741823)₁₀


What is the largest 2's complement 30-bit binary number?

- ☐ (536870912)₁₀
- ☒ (536870911)₁₀
- ☐ (2147483647)₁₀
- ☐ (2147483648)₁₀

What is the complement of the Boolean expression $AB(B'C + AC)$?

- ☒ $(A' + B') + (B + C')(A' + C')$
- ☒ $(A' + B') + ((B'C)')(AC)'$
- ☐ $(A + B)(B' + C)(A + C)$
- ☐ $(A' + B')(B + C') + (A + C')$

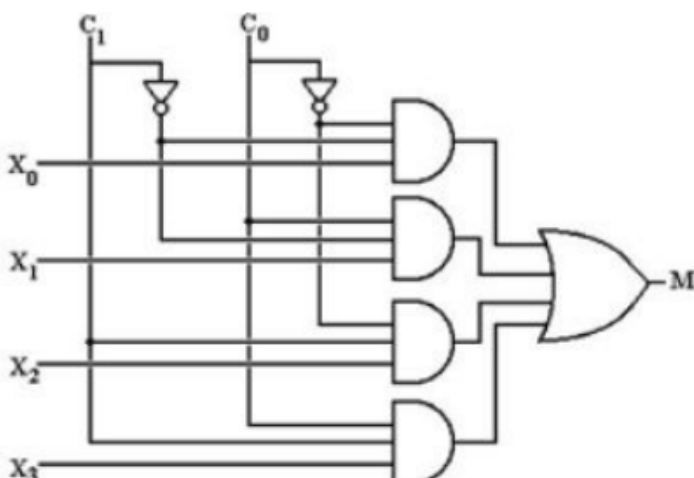In the following combinational circuit, what is the output at M with $C_1 = 1$ and $C_0 = 0$?



- ☐ x_0
- ☐ x_1
- ☒ x_2
- ☐ x_3

$(A \text{ xor } B) \text{ xor } B = ?$

- ☐ All ones
- ☐ All zeros
- ☒ A
- ☐ B


Half Adder combinational circuit requires _____

- ☐ two binary inputs.
- ☐ two binary outputs.
- ☒ both two binary inputs and two binary outputs.
- ☐ none of the above.

Combinational circuits do not have _____.


- ☐ gates
- ☒ memory elements
- ☐ power source
- ☐ none of the alternatives are correct

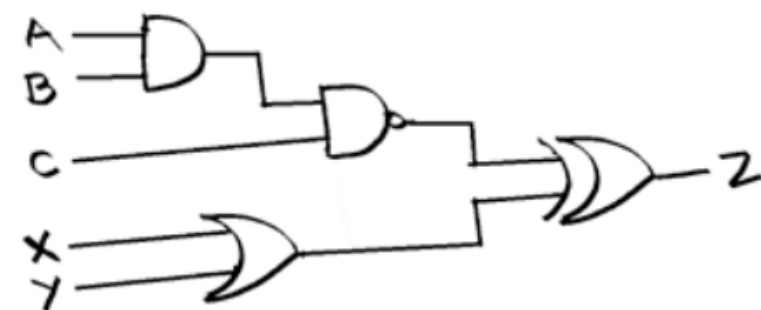Each gate of the following circuit has a propagation delay of 100 picoseconds and a contamination delay of 50 picoseconds. What is the contamination delay of the circuit?



- ☐ 50 picoseconds
- ☒ 100 picoseconds
- ☐ 150 picoseconds
- ☐ 200 picoseconds

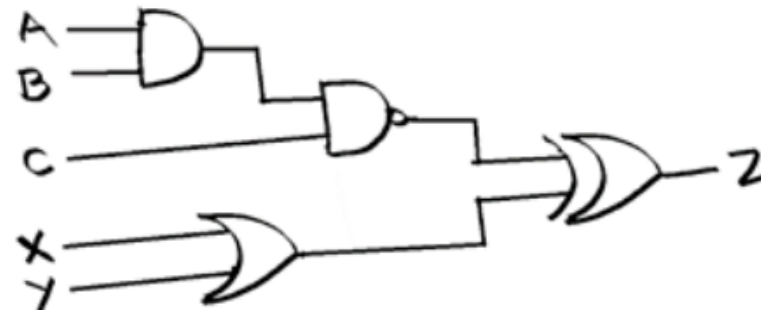Each gate of the following circuit has a propagation delay of 100 picoseconds and a contamination delay of 50 picoseconds. What is the propagation delay of the circuit?



- ☐ 100 picoseconds
- ☐ 200 picoseconds
- ☒ 300 picoseconds
- ☐ 400 picoseconds