End Semester Examination, Autumn-2021-22

Part-B Full marks: 20 Exam duration: 1 Hours

Answer all questions. Figures next to each question in square bracket indicate marks.

All Parts of a question should be answered at one place.


This question paper contains ONE page.

1. Your roll number has the pattern 1yyCSabcd. Count all unique digits in {a, b, c, d}. If the number of unique digits are less than 4, take any digit of your choice to make 4 unique digits. Consider the final 4 unique digits as your minterms and let it be {p, q, r, s}.

Use T-Flip-Flops to design a 4-bit counter that has a control input called \overline{F}/R . The functionality of the control input is given below. [10]

$$\overline{F}/R = \begin{cases} 0, & \text{the circuit counts in Forward sequence as } \mathbf{p} \to \mathbf{q} \to \mathbf{r} \to \mathbf{s} \to \mathbf{p} \cdots \\ 1, & \text{the circuit counts in Reverse sequence as } \mathbf{s} \to \mathbf{r} \to \mathbf{q} \to \mathbf{p} \to \mathbf{s} \cdots \end{cases}$$

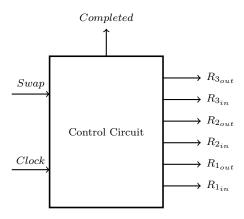2. Design the <u>control circuit</u> to swap the contents of two n-bit registers R_1 and R_2 . Let there be a temporary n-bit register R_3 . The following figure indicates the external signals involved in the control circuit.



The swap procedure begins when Swap = 1. The swap procedure has the following sequence along with the control signals —

$$\begin{split} [R_3] \leftarrow [R_2] & \qquad R_{3_{in}} = 1, \ R_{2_{out}} = 1 \\ [R_2] \leftarrow [R_1] & \qquad R_{2_{in}} = 1, \ R_{1_{out}} = 1 \\ [R_1] \leftarrow [R_3] & \qquad R_{1_{in}} = 1, \ R_{3_{out}} = 1 \end{split}$$

Once the Swap signal has been asserted, the above three steps are executed irrespective of subsequent Swap signals, and finally Completed signal becomes high to indicate that the swap procedure has been completed. In your design, include state diagram, state table, logic diagram along with excitation equations. [10]

##