End Semester Examination, Autumn-2020-21 Part-B

Full marks: 20 Exam duration: 1 Hours

Answer all questions. Figures next to each question in square bracket indicate marks.

All Parts of a question should be answered at one place.

This question paper contains ONE page.

1. Use a $2^{n-1} \times 1$ MUX (with *n* variables logic) to design a combinational circuit for the function $F = \sum (Minterms)$. [5]

The minterms are to be generated in the following way:

- Take the last 3 digits of your roll number and square it.
- Consider any 5 unique digits in the result as the minterms.
- If the number of unique digits are less than 5, append some more unique digits of your choice to make 5 unique terms.
- 2. Design a synchronous counter to count the minterm sequence generated for the above question from LSB to MSB. [5]
- 3. Design a sequence generator to generate a pattern.

[10]

The format of the pattern is given below:

- Take the last 3 digits of your roll number and convert it to binary.
- Use 4 least significant bits of the binary number.
- If you get all ones, replace the LSB with 0.

The resultant binary number is your pattern.