



Gate-Level Minimization

By:

Ratnakar Dash

August 17, 2022







Table of Contents

- 1** Introduction to Gate-Level Minimization
- 2** The Map Method
- 3** Don't-Care Conditions
- 4** EXCLUSIVE-OR FUNCTION
- 5** HARDWARE DESCRIPTION LANGUAGE

Gate-Level Minimization

1

2

3

4

5

- Gate-level minimization is the design task of finding an optimal gate-level implementation of the Boolean functions describing a digital circuit

The Map Method

1

2

3

4

5

- The complexity of the digital logic gates that implement a Boolean function is directly related to the complexity of the algebraic expression from which the function is implemented.
- The map method presented here provides a simple, straightforward procedure for minimizing Boolean functions. This method may be regarded as a pictorial form of a truth table. The map method is also known as the Karnaugh map or K-map .

The Map Method (contd.)

1

2

3

4

5

- The complexity of the digital logic gates
 - ◆ the complexity of the algebraic expression
- Logic minimization
 - ◆ algebraic approaches: lack specific rules
 - ◆ the Karnaugh map (or K-map)
 - a simple straight forward procedure
 - a pictorial form of a truth table
 - applicable if the number of variables < 7
- A diagram made up of squares
 - ◆ each square represents one minterm.

Boolean function

1

2

3

4

5

Boolean function

- sum of minterms
- sum of products (or product of sum) in the simplest form
- a minimum number of terms
- a minimum number of literals
- The simplified expression may not be unique

Two-Variable Map

Two-Variable Map

A two-variable map

- four minterms
- $x' = \text{row } 0$; $x = \text{row } 1$
- $y' = \text{column } 0$;
 $y = \text{column } 1$
- a truth table in square diagram
- xy
- $x+y =$

m_0	m_1
m_2	m_3

(a)

y	
$\overbrace{\hspace{1cm}}$	
$x \backslash y$	$\begin{matrix} 0 & 1 \end{matrix}$
$\begin{matrix} 0 \\ 1 \end{matrix}$	$\begin{matrix} m_0 & m_1 \\ x'y' & x'y \\ m_2 & m_3 \\ xy' & xy \end{matrix}$

(b)

FIGURE 3.1

Two-variable K-map

y	
$\overbrace{\hspace{1cm}}$	
$x \backslash y$	$\begin{matrix} 0 & 1 \end{matrix}$
$\begin{matrix} 0 \\ 1 \end{matrix}$	$\begin{matrix} m_0 & m_1 \\ m_2 & m_3 \end{matrix}$

y	
$\overbrace{\hspace{1cm}}$	
$x \backslash y$	$\begin{matrix} 0 & 1 \end{matrix}$
$\begin{matrix} 0 \\ 1 \end{matrix}$	$\begin{matrix} m_0 & m_1 \\ m_2 & m_3 \end{matrix}$

Three-Variable Map

- eight minterms
- the Gray code sequence
- any two adjacent squares in the map differ by only one variable
 - primed in one square and unprimed in the other
 - e.g. m_5 and m_7 can be simplified
 - $m_5 + m_7 = xy'z + xyz = xz (y' + y) = xz$

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

(a)

		y			
		00	01	11	10
x \ yz	0	m_0 $x'y'z'$	m_1 $x'y'z$	m_3 $x'yz$	m_2 $x'yz'$
	1	m_4 $xy'z'$	m_5 $xy'z$	m_7 xyz	m_6 xyz'
		z			

(b)

FIGURE 3.3
Three-variable K-map

Example

Example 3-1

- $F(x,y,z) = \Sigma(2,3,4,5)$
- $F = x'y + xy'$

 


FIGURE 3.4

Map for Example 3.1, $F(x,y,z) = \Sigma(2,3,4,5) = x'y + xy'$

Example (Cont...)

- m_0 and m_2 (m_4 and m_6) are adjacent
- $m_0 + m_2 = x'y'z' + x'yz' = x'z' (y' + y) = x'z'$
- $m_4 + m_6 = xy'z' + xyz' = xz' (y' + y) = xz'$

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

(a)

		y			
		yz	00	01	11
x	0	m_0 $x'y'z'$	m_1 $x'y'z$	m_3 $x'yz$	m_2 $x'yz'$
	1	m_4 $xy'z'$	m_5 $xy'z$	m_7 xyz	m_6 xyz'
		z			

(b)

FIGURE 3.3

Three-variable K-map

Example (Cont...)

Example 3-2

■ $F(x,y,z) = \Sigma(3,4,6,7) = yz + xz'$

 


FIGURE 3.5

Map for Example 3.2, $F(x,y,z) = \Sigma(3,4,6,7) = yz + xz'$

Four adjacent squares

■ 2, 4, 8 and 16 squares

$$\begin{aligned} \blacksquare m_0 + m_2 + m_4 + m_6 &= x'y'z' + x'yz' + xy'z' + xyz' \\ &= x'z'(y' + y) + xz'(y' + y) \\ &= x'z' + xz' = z' \end{aligned}$$

$$\begin{aligned} \blacksquare m_1 + m_3 + m_5 + m_7 &= x'y'z + x'yz + xy'z + xyz \\ &= x'z(y' + y) + xz(y' + y) \\ &= x'z + xz = z \end{aligned}$$

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

(a)

		yz			
		00	01	11	10
x	0	m_0 $x'y'z'$	m_1 $x'y'z$	m_3 $x'yz$	m_2 $x'yz'$
	1	m_4 $xy'z'$	m_5 $xy'z$	m_7 xyz	m_6 xyz'

z

(b)

FIGURE 3.3

Three-variable K-map

Gate-Level Minimization 3-10

Example 3-3

- $F(x,y,z) = \Sigma(0,2,4,5,6)$
- $F = z' + xy'$

 


FIGURE 3.6

Map for Example 3.3, $F(x,y,z) = \Sigma(0,2,4,5,6) = z' + xy'$

Example 3-4

- $F = A'C + A'B + AB'C + BC$
- express it in sum of minterms
- find the minimal sum of products expression

 


FIGURE 3.7

Map of Example 3.4, $A'C + A'B + AB'C + BC = C + A'B$

1

2

3

4


5

Four-Variable Map

- 16 minterms
- combinations of 2, 4, 8, and 16 adjacent squares

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6
m_{12}	m_{13}	m_{15}	m_{14}
m_8	m_9	m_{11}	m_{10}


(a)

 

(b)

 Example

■ $F(w,x,y,z) = \Sigma(0,1,2,4,5,6,8,9,12,13,14)$



■ $F = y' + w'z' + xz'$

Note: $w'y'z' + w'yz' = w'z'$
 $xy'z' + xyz' = xz'$

FIGURE 3.9

Map for Example 3.5, $F(w, x, y, z) = \Sigma(0,1, 2, 4, 5, 6, 8, 9, 12, 13, 14) = y' + w'z' + xz'$

1

2


3

4

5

Simplify the Boolean function

$$F = A'B'C' + B'CD' + A'B'CD' + AB'C'$$

 

Note: $A'B'C'D' + A'B'CD' = A'B'D'$
 $AB'C'D' + AB'CD' = AB'D'$
 $A'B'D' + AB'D' = B'D'$
 $A'B'C' + AB'C' = B'C'$

Note: $A'B'C'D' + A'B'CD' = A'B'D'$
 $AB'C'D' + AB'CD' = AB'D'$
 $A'B'D' + AB'D' = B'D'$
 $A'B'C' + AB'C' = B'C'$

FIGURE 3.10

Map for Example 3.6, $A'B'C' + B'CD' + A'B'CD' + AB'C' = B'D' + B'C' + A'CD'$

Prime Implicants

1

2

3

4

5

- all the minterms are covered
- minimize the number of terms
- a prime implicant: a product term obtained by combining the maximum possible number of adjacent squares (combining all possible maximum numbers of squares)
- essential: a minterm is covered by only one prime implicant
- the essential P.I. must be included

1

2

3


4

5

 Example


Consider $F(A,B,C,D) = \sum (0,2,3,5,7,8,9,10,11,13,15)$

- the simplified expression may not be unique
- $F = BD + B'D' + CD + AD = BD + B'D' + CD + AB'$
 $= BD + B'D' + B'C + AD = BD + B'D' + B'C + AB'$



Note: $A'B'C'D' + A'B'CD' = A'B'D'$
 $AB'C'D' + AB'CD' = AB'D'$
 $A'B'D' + AB'D' = B'D'$

 (a) Essential prime implicants
 BD and $B'D'$



(b) Prime implicants CD , $B'C$,
 AD , and AB'

Five-Variable Map

1

2

3

4

5

Inverse

- Map for more than four variables becomes complicated
- five-variable map: two four-variable map (one on the top of the other)

1

2



3

4

5

Five-Variable Map

  
$$F = \Sigma(0,2,4,6,9,13,21,23,25,29,31)$$



Map for Example 3-7; $F = A'B'E' + BD'E + ACE$

$$F = A'B'E' + BD'E + ACE$$

Example

 

Product of Sums Simplification

■ Approach 1

- Simplified F' in the form of sum of products
- Apply DeMorgan's theorem $F = (F')'$
- F' : sum of products $\Rightarrow F$: product of sums

■ Approach 2: duality

- combinations of maxterms (it was minterms)
- $M_0 M_1 = (A+B+C+D)(A+B+C+D')$
 $= (A+B+C)+(DD')$
 $= A+B+C$

	CD			
AB	00	01	11	10
00	M_0	M_1	M_3	M_2
01	M_4	M_5	M_7	M_6
11	M_{12}	M_{13}	M_{15}	M_{14}
10	M_8	M_9	M_{11}	M_{10}

1

2

3

4

5

Example

Example 3-7

■ $F = \Sigma(0,1,2,5,8,9,10)$

 


FIGURE 3.12

Map for Example 3.7, $F(A, B, C, D) = \Sigma(0, 1, 2, 5, 8, 9, 10) = B'D' + B'C' + A'C'D = (A' + B')(C' + D')(B' + D)$

Note: $BC'D' + BCD' = BD'$

- $F' = AB + CD + BD'$
- Apply DeMorgan's theorem; $F = (A' + B')(C' + D')(B' + D)$
- Or think in terms of maxterms

1

2


3

4


5

 Example

- Gate implementation of the function of Example 3-7



(a) $F = B'D' + B'C' + A'C'D$

 

(b) $F = (A' + B')(C' + D')(B' + D)$

1

2

3

4

5

Example

Consider the function defined in Table 3.1.

In sum-of-minterm:

$$F(x, y, z) = \sum(1, 3, 4, 6)$$

In sum-of-maxterm:

$$F'(x, y, z) = \Pi(0, 2, 5, 7)$$

Taking the complement of F'

$$F(x, y, z) = (x' + z')(x + z)$$

Table 3.1

Truth Table of Function F

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

1

2

3

4

5

Example

Consider the function defined in Table 3.1.

Combine the 1's:

$$F(x, y, z) = x'z + xz'$$

Combine the 0's :

$$F(x, y, z) = xz + x'z'$$

		y			
		00	01	11	10
x	0	m_0 0	m_1 1	m_3 1	m_2 0
	1	m_4 1	m_5 0	m_7 0	m_6 1

Annotations:
 - A horizontal group of 1s in the top row (m_1, m_3) and bottom row (m_4, m_6) is labeled $x'z$.
 - A vertical group of 1s in the first column (m_1, m_4) and third column (m_3, m_7) is labeled xz' .
 - The columns are grouped by z (00, 01) and z' (11, 10).

1

2

3

4

5

Inverse

- The value of a function is not specified for certain combinations of variables
- BCD; 1010-1111: don't care
- The don't care conditions can be utilized in logic minimization (can be implemented as 0 or 1)
- Example 3-8
 - ◆ $F(w, x, y, z) = \sum(1, 3, 7, 11, 15)$
 - ◆ $d(w, x, y, z) = \sum(0, 2, 5)$

1

2

3

4

5

Example

- Figure 3.15(a) : $F = yz + w'x'$
- Figure 3.15(b) : $F = yz + w'z$
- $F = \Sigma(0,1,2,3,7,11,15)$; $F = \Sigma(1,3,5,7,11,15)$
- either expression is acceptable

		y			
		00	01	11	10
$w'x'$	00	m_0 X	m_1 1	m_3 1	m_2 X
	01	m_4 0	m_5 X	m_7 1	m_6 0
	11	m_{12} 0	m_{13} 0	m_{15} 1	m_{14} 0
w	10	m_8 0	m_9 0	m_{11} 1	m_{10} 0
		z			

x

yz

(a) $F = yz + w'x'$

		y			
		00	01	11	10
$w'x'$	00	m_0 X	m_1 1	m_3 1	m_2 X
	01	m_4 0	m_5 X	m_7 1	m_6 0
	11	m_{12} 0	m_{13} 0	m_{15} 1	m_{14} 0
w	10	m_8 0	m_9 0	m_{11} 1	m_{10} 0
		z			



x

yz

  (b) $F = yz + w'z$

NAND and NOR Implementation

- NAND gate is a universal gate
- can implement any digital system



1

2

3

4


5

Example

Two graphic symbols for a NAND gate



(a) AND-invert

 

(b) Invert-OR

1

2


3

4


5

Two-level Implementation

 
- two-level logic
- NAND-NAND = sum of products
- Example: $F = AB + CD$
- $F = ((AB)' (CD)')' = AB + CD$



(a)

 

(b)

 

(c)

1

2

3




4

5

Example

$$F(x, y, z) = \sum(1, 2, 3, 4, 5, 7)$$

$$F(x, y, z) = xy' + x'y + z$$

   

1

2

3

4

5

The procedure

- simplified in the form of sum of products
- a NAND gate for each product term; the inputs to each NAND gate are the literals of the term
- a single NAND gate for the second sum term
- A single literal requires an inverter in the first level

1

2

3

4

5

Multilevel NAND Circuits

- Boolean function implementation
- AND-OR logic \implies NAND-NAND logic
- AND \implies NAND + inverter
- OR: inverter + OR = NAND

1


2

3


4

5

Example

 

(a) AND-OR gates

 

(b) NAND gates

FIGURE 3.20

Implementing $F = A(CD + B) + BC'$

1


2

3


4

5

Example

 

(a) AND-OR gates

 

(b) NAND gates

FIGURE 3.21

Implementing $F = (AB' + A'B)(C + D')$

1

2

3

4

5

NOR Implementation

- NOR function is the dual of NAND function
- The NOR gate is also universal

1


2

3

4

5

Example

 

Two graphic symbols for a NOR gate

 
 


FIGURE 3.23

Two graphic symbols for the NOR gate

Example: $F = (A + B)(C + D)E$

 


FIGURE 3.24

Implementing $F = (A + B)(C + D)E$

1

2

3

4

5

Two graphic symbols for a NOR gate

Example: $F = (AB' + A'B)(C + D')$

 


FIGURE 3.25

Implementing $F = (AB' + A'B)(C + D')$ with NOR gates

1

2

3

4

5

Wired logic

- a wire connection between the outputs of two gates
- open-collector TTL NAND gates: wired-AND logic
- the NOR output of ECL gates: wired-OR logic

1

2

3

4

5


Other Two-level Implementations

$$F = (AB)' \cdot (CD)' = (AB + CD)' = (A' + B')(C' + D')$$

AND-OR-INVERT function


$$F = (A + B)' + (C + D)' = [(A + B)(C + D)]'$$

OR-AND-INVERT function

 

(a) Wired-AND in open-collector
TTL NAND gates.

(AND-OR-INVERT)

 

(b) Wired-OR in ECL gates

(OR-AND-INVERT)

1

2

3

4

5

Nondegenerate Forms

- 16 possible combinations of two-level forms
- The eight nondegenerate forms
 - ◆ AND-OR, OR-AND, NAND-NAND, NOR-NOR, NOR-OR, NAND-AND, OR-AND, AND-OR
 - ◆ AND-OR and NAND-NAND = sum of products
 - ◆ OR-AND and NOR-NOR = product of sums
 - ◆ NOR-OR, NAND-AND, OR-AND, AND-OR = ?

1

2

3

4

5

AND-OR-Invert Implementation

- AND-OR-INVERT (AOI) Implementation
 - ◆ $\text{NAND-AND} = \text{AND-NOR} = \text{AOI}$
 - ◆ $F = (AB + CD + E)'$
 - ◆ $F' = AB + CD + E$ (sum of products)

1


2

3


4

5


AND-OR-Invert Implementation

 

(a) AND-NOR

 

(b) AND-NOR

 

(c) NAND-AND

FIGURE 3.27

AND-OR-INVERT circuits, $F = (AB + CD + E)'$

1

2

3

4

5

OR-AND-INVERT (OAI) Implementation

- OR-AND-INVERT (OAI) Implementation
 - ◆ OR-NAND = NOR-OR = OAI
 - ◆ $F = ((A+B)(C+D)E)'$
 - ◆ $F' = (A+B)(C+D)E$ (product of sums)

1

2

3

4

5

OR-AND-INVERT (OAI) Implementation

 


FIGURE 3.28

OR-AND-INVERT circuits, $F = [(A + B)(C + D)E]'$

1

2

3

4

5

Tabular Summary and Examples

Table 3.2
Implementation with Other Two-Level Forms

Equivalent Nondegenerate Form		Implements the Function	Simplify F' into	To Get an Output of
(a)	(b)*			
AND-NOR	NAND-AND	AND-OR-INVERT	Sum-of-products form by combining 0's in the map.	F
OR-NAND	NOR-OR	OR-AND-INVERT	Product-of-sums form by combining 1's in the map and then complementing.	F

*Form (b) requires an inverter for a single literal term.

1

2

3

4

5

Example

- $F' = x'y + xy' + z$ (F': sum of products)
- $F = (x'y + xy' + z)'$ (F: AOI implementation)

- $F = x'y'z' + xyz'$ (F: sum of products)
- $F' = (x+y+z)(x'+y'+z)$ (F': product of sums)
- $F = ((x+y+z)(x'+y'+z))'$ (F: OAI)

Example

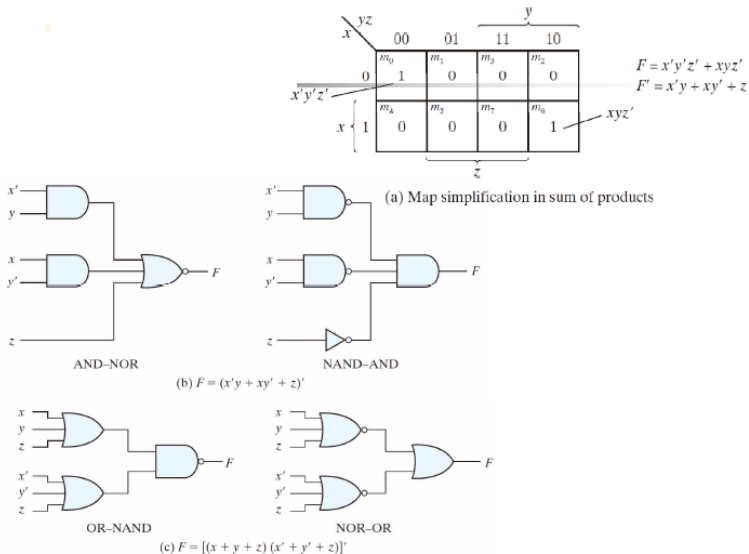


FIGURE 3.29

Other two-level implementations

1

2

3

4

5

EXCLUSIVE-OR FUNCTION

The exclusive-OR (XOR), denoted by the symbol \oplus , is a logical operation that performs the following Boolean operation:

$$x \oplus y = xy' + x'y$$


The exclusive-OR is equal to 1 if only x is equal to 1 or if only y is equal to 1 (i.e., x and y differ in value), but not when both are equal to 1 or when both are equal to 0. The exclusive-NOR, also known as equivalence, performs the following Boolean operation:

$$(x \oplus y)' = xy + x'y'$$


The exclusive-NOR is equal to 1 if both x and y are equal to 1 or if both are equal to 0. The exclusive-NOR can be shown to be the complement of the exclusive-OR by means of a truth table or by algebraic manipulation:

$$(x \oplus y)' = (xy' + x'y)' = (x' + y)(x + y') = xy + x'y'$$

Example

 

(a) Exclusive-OR with AND-OR-NOT gates

 

(b) Exclusive-OR with NAND gates

FIGURE 3.30
Exclusive-OR implementations

1

2

3

4

5

Odd function

- The exclusive-OR operation with three or more variables can be converted into an ordinary Boolean function by replacing the \oplus symbol with its equivalent Boolean expression.

$$\begin{aligned}A \oplus B \oplus C &= (AB' + A'B)C' + (AB + A'B')C \\&= AB'C' + A'BC' + ABC + A'B'C \\&= \Sigma(1, 2, 4, 7)\end{aligned}$$

$$\begin{aligned}
 A \oplus B \oplus C \oplus D &= (AB' + A'B) \oplus (CD' + C'D) \\
 &= (AB' + A'B)(CD + C'D') + (AB + A'B')(CD' + C') \\
 &= \Sigma(1, 2, 4, 7, 8, 11, 13, 14)
 \end{aligned}$$

BC		B			
		00	01	11	10
A	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6
			1		1
		1		1	


(a) Odd function $F = A \oplus B \oplus C$

BC		B			
		00	01	11	10
A	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6
		1		1	
			1		1


(b) Even function $F = (A \oplus B \oplus C)'$

FIGURE 3.31

 Map for a three-variable exclusive-OR function



(a) 3-input odd function

 

(b) 3-input even function

FIGURE 3.32

Logic diagram of odd and even functions

1

2

3

4

5

Example

AB \ CD		C			
		00	01	11	10
A	00	m_0	m_1	m_3	m_2
	01	m_4	m_5	m_7	m_6
	11	m_{12}	m_{13}	m_{15}	m_{14}
	10	m_8	m_9	m_{11}	m_{10}
		D			

Map for the odd function $F = A \oplus B \oplus C \oplus D$. The function is 1 for minterms $m_1, m_2, m_4, m_5, m_7, m_8, m_9, m_{10}, m_{12}, m_{13}, m_{14}, m_{15}$.

(a) Odd function $F = A \oplus B \oplus C \oplus D$

AB \ CD		C			
		00	01	11	10
A	00	m_0	m_1	m_3	m_2
	01	m_4	m_5	m_7	m_6
	11	m_{12}	m_{13}	m_{15}	m_{14}
	10	m_8	m_9	m_{11}	m_{10}
		D			

Map for the even function $F = (A \oplus B \oplus C \oplus D)'$. The function is 1 for minterms $m_0, m_3, m_6, m_7, m_{10}, m_{11}, m_{14}, m_{15}$.

(b) Even function $F = (A \oplus B \oplus C \oplus D)'$

FIGURE 3.33

Map for a four-variable exclusive-OR function

1

2

3

4

5

Parity Generation and Checking


- The exclusive-OR operation with three or more variables can be converted into an ordinary Boolean function by replacing the \oplus symbol with its equivalent Boolean expression.

Example


Table 3.3

Even-Parity-Generator Truth Table

Three-Bit Message			Parity Bit
x	y	z	P
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 

(a) 3-bit even parity generator

 

(b) 4-bit even parity checker

1

2

3

4

5

HARDWARE DESCRIPTION LANGUAGE

- A hardware description language (HDL) is a computer-based language that describes the hardware of digital systems in a textual form.
- It resembles an ordinary computer programming language, such as C, but is specifically oriented to describing hardware structures and the behavior of logic circuits.
- It can be used to represent logic diagrams, truth tables, Boolean expressions, and complex abstractions of the behavior of a digital system.

1

2

3

4

5

 


FIGURE 3.35

Circuit to demonstrate an HDL

1

2

3

4

5

HDL Example 3.1 (Combinational Logic Modeled with Primitives)

// Verilog model of circuit of Figure 3.35. IEEE 1364–1995 Syntax

```
module Simple_Circuit (A, B, C, D, E);  
    output      D, E;  
    input       A, B, C;  
    wire        w1;  
  
    and         G1 (w1, A, B); // Optional gate instance name  
    not         G2 (E, C);  
    or          G3 (D, w1, E);  
endmodule
```

1

2

3

4

5

Table 3.5
Output of Gates after Delay

	Time Units (ns)	Input	Output		
		ABC	E	w1	D
Initial	—	0 0 0	1	0	1
Change	—	1 1 1	1	0	1
	10	1 1 1	0	0	1
	20	1 1 1	0	0	1
	30	1 1 1	0	1	0
	40	1 1 1	0	1	0
	50	1 1 1	0	1	1

1

2

3

4

5

Gate Delays

HDL Example 3.2 (Gate-Level Model with Propagation Delays)

// Verilog model of simple circuit with propagation delay

```
module Simple_Circuit_prop_delay (A, B, C, D, E);  
    output D, E;  
    input  A, B, C;  
    wire   w1;  
  
    and          #(30) G1 (w1, A, B);  
    not          #(10) G2 (E, C);  
    or           #(20) G3 (D, w1, E);  
endmodule
```

1

2

3

4

5

Gate Delays

HDL Example 3.3 (Test Bench)

// Test bench for Simple_Circuit_prop_delay

```
module t_Simple_Circuit_prop_delay;
```

```
  wire  D, E;
```

```
  reg    A, B, C;
```

```
  Simple_Circuit_prop_delay M1 (A, B, C, D, E); // Instance name required
```

```
  initial
```

```
  begin
```

```
    A = 1'b0; B = 1'b0; C = 1'b0;
```

```
    #100 A = 1'b1; B = 1'b1; C = 1'b1;
```

```
  end
```

```
  initial #200 $finish;
```

```
endmodule
```

1

2

3

4

5

Gate Delays

 


FIGURE 3.36

Simulation output of HDL Example 3.3

1

2

3

4

5

Gate Delays

HDL Example 3.4 (Combinational Logic Modeled with Boolean Equations)

// Verilog model: Circuit with Boolean expressions

```
module Circuit_Boolean_CA (E, F, A, B, C, D);
```

```
    output      E, F;
```

```
    input       A, B, C, D;
```

```
    assign E = A || (B && C) || ((!B) && D);
```

```
    assign F = ((!B) && C) || (B && (!C) && (!D));
```

```
endmodule
```

1

2

3

4

5

User-Defined Primitives

- The logic gates used in Verilog descriptions with keywords and, or, etc., are defined by the system and are referred to as system primitives.
- The user can create additional primitives by defining them in tabular form. These types of circuits are referred to as user-defined primitives (UDPs).

1

2

3

4

5

User-Defined Primitives

 


FIGURE 3.37

Schematic for *Circuit with_UDP_02467*

References I

- [1] M. M. Mano and M. D. Ciletti, *Digital Design (4th Edition)*. USA: Prentice-Hall, Inc., 2006.

*Thank
you!*

The text "Thank you!" is written in a black, elegant cursive script. It is surrounded by thin, light gray decorative swirls and flourishes. At the bottom of the image, there is a solid black horizontal bar with a small white triangular notch on the left side.