

NATIONAL INSTITUTE OF TECHNOLOGY ROURKELA

MID-TERM EXAMINATION, 2018

BTech 3rd Semester

SUBJECT: Digital System Design

FULL MARKS: 30


DEPT. CODE: CS 2001

Duration of Examination: 2Hours

Number of pages: 1

Answer **Any FIVE**. Figures at the right hand margin indicate marks

All parts of a question should be answered at one place

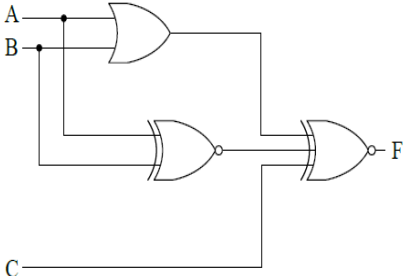Q.No.	Question	Marks
1	<p>(a) Implement the function $F(A, B, C, D) = \Sigma(1, 3, 4, 11, 12, 13, 14, 15)$ using an 8 X 1 multiplexer.</p> <p>(b) What is the minimum number of 2 input NAND gates required to implement the function $F = (X' + Y')(Z + W)$?</p> <p>(c) Show that $(X + Y' + XY)(X + Y')(X'Y) = 0$</p>	[3+2+1]
2	<p>(a) Design an Octal to Binary Encoder.</p> <p>(b) Find the octal equivalent of $(378.93)_{10}$</p>	[4+2]
3	<p>(a) What do you mean by race around condition? How to deal with it?</p> <p>(b) Convert $F = A(B + C')$ to Maxterms.</p> <p>(c) A locker has been rented in the bank. Express the process of opening the locker in terms of digital operation.</p>	[2+2+2]
4.	<p>(a) What will be the input combination for the output F to be 1 in the logic circuit shown below? Justify your answer.</p>  <p>(b) State the limitations of Karnaugh map.</p> <p>(c) Explain address and word in association with ROM with a diagram.</p>	[2+2+2]
5	<p>(a) Design a 2-bit Magnitude Comparator.</p> <p>(b) Convert $(A0F9.0EB)_{16}$ to decimal.</p>	[4+2]
6.	<p>(a) Given the two binary numbers $X = 1010100$ and $Y = 1000011$, perform the subtraction of (a) $X - Y$ and (b) $Y - X$ using 2's complements.</p> <p>(b) A Boolean function f of two variables X and Y is defined as follows: $f(0, 0) = f(0, 1) = f(1, 1) = 1$; $f(1, 0) = 0$ Assuming complements of X and Y are not available, Find the minimum cost solution for realizing using only 2-input NOR gates and 2-input OR gates (each having cost=1). What would have the total cost?</p>	[3+3]

